

1 DC Motor shunt connected


1 DC Gen. Separately excited (mech. coupled to motor.)

$$R_a = 0.8 \Omega, L_a = 12.5 \text{ mH} = L_a$$

$$220 \text{ V}, 23.4 \text{ A}, 1500 \text{ RPM}$$

$$R_{sh} = 210 \Omega, L_{sh} = 23 \text{ H}$$
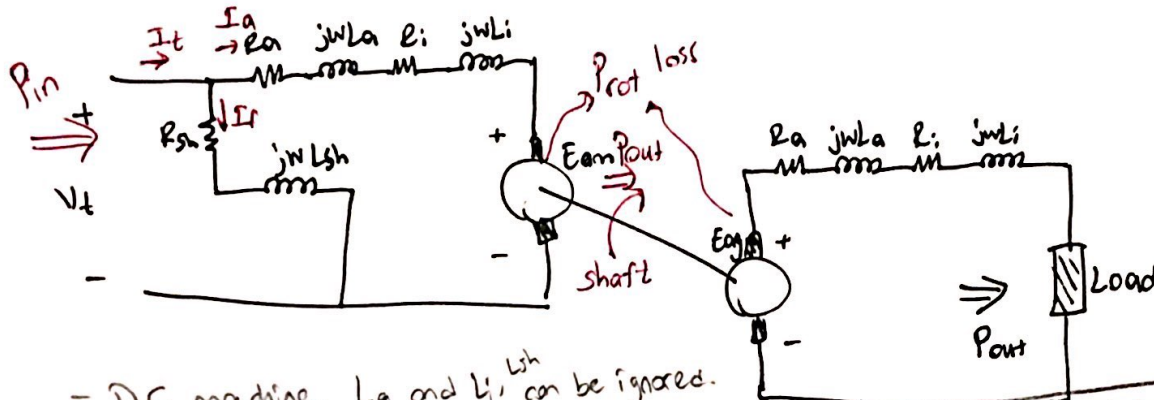
$$R_i = 0.27 \Omega, L_i = 12 \text{ mH}$$



- DC machine. L_a and L_i can be ignored.
- Assume machine is working at rated conditions.

- Assume rotational losses are 200W.

$$V_t = 220 \text{ V}, I_t = 23.4 \text{ A}, P_{in} = 5148 \text{ W}$$

$$I_f = \frac{V_t}{R_{sh}} = \frac{220}{210} = 1.0476 \text{ A}$$

$$\Rightarrow I_a = I_t - I_f = 22.3524 \text{ A}$$

$$P_{\text{field-loss}} = I_f^2 R_{sh} = 230 \text{ W}$$

$$E_{cm} = V_t - I_a(R_a + R_i) = 220 - 22.3524(0.8 + 0.27)$$

$$E_{cm} = 196 \text{ V} \leftarrow \text{Induced Voltage at the motor side. (at rated conditions)}$$

$$P_{out} = E_{cm} I_a - P_{rot, loss} = 196 \times (22.3524) - 200 = 4181 \text{ W}$$

$$P_{in}(\text{generator}) = P_{out} - 200 \text{ W (assumed)} = 4181 - 200 = 3981 \text{ W}$$

- After this part, voltage induced over the generator affects the output power. It also affects the current passing through the circuit. Now, assume E_{cg} (voltage induced over generator) is 190 V.

$$P_{in}(\text{generator}) = 3981 = E_{cg} \cdot I_{ag} = 190 \cdot I_{ag} \Rightarrow I_{ag} = 20.95 \text{ A}$$

$$P_{out} = (E_{cg} - (R_a + R_i) I_{ag}) \times I_{ag} = (190 - 1.07 \times 20.95) \times 20.95 = 3510.8 \text{ W}$$

$$\eta_g = \frac{P_{out}}{P_{in} + P_{\text{field-loss}}} = \frac{3510.8}{4181 + 230} \times 100 = 79 \%$$

→ $P_{\text{field-loss}}$ is added because generator is field excited and it didn't draw in the schematic above.